

**Chapter 9, Problem 20.**

A linear network has a current input  $7.5\cos(10t+30^\circ)$  A and a voltage output  $120\cos(10t+75^\circ)$  V. Determine the associated impedance.