## Chapter 7, Problem 7.

Assume that the switch in Fig. 7.87 has been in position A for a long time and is moved to position B at t=0. Then at t = 1 second, the switch moves from B to C. Find  $v_C(t)$  for t 0.

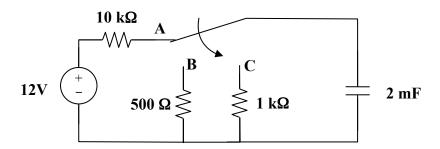


Figure 7.87 For Prob. 7.7.