

Chapter 10, Problem 15.

Solve for the current \mathbf{I} in the circuit of Fig. 10.64 using nodal analysis.

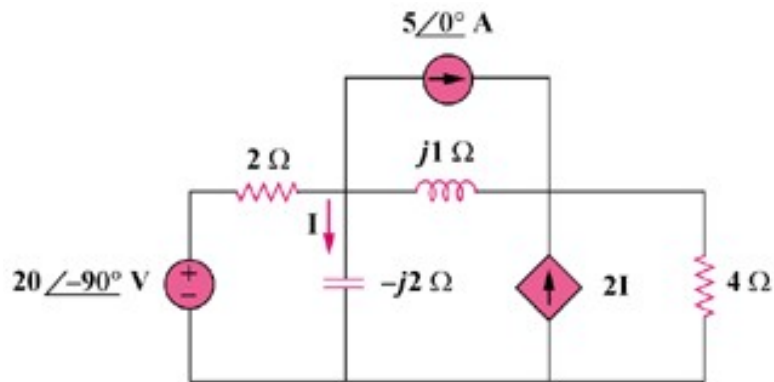


Figure 10.64
For Probs. 10.15 and 10.33.