

**Chapter 11, Problem 96.**

A power amplifier has an output impedance of  $40 + j8\Omega$ . It produces a no-load output voltage of 146 V at 300 Hz.

- (a) Determine the impedance of the load that achieves maximum power transfer.
- (b) Calculate the load power under this matching condition.