

Chapter 11, Problem 13.

The Thevenin impedance of a source is $Z_{Th} = 120 + j60 \, \Omega$, while the peak Thevenin voltage is $V_{Th} = 165 + j0 \, \text{V}$. Determine the maximum available average power from the source.