

11Equation Section 1 **Chapter 7, Problem 9.**

The switch in Fig. 7.89 opens at  $t=0$ . Find  $v_o$  for  $t > 0$ .

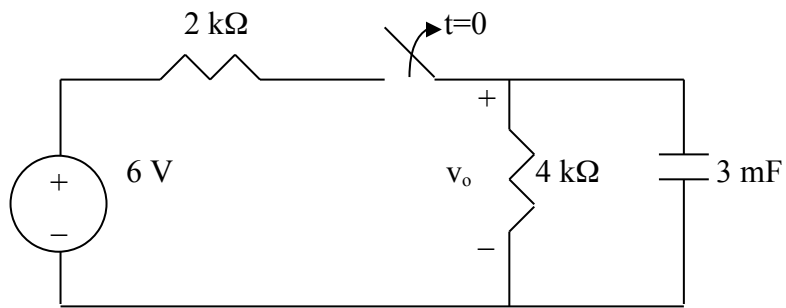


Figure 7.89  
For Prob. 7.9.