

**Chapter 5, Problem 43**

A four-input summing amplifier has  $R_1 = R_2 = R_3 = R_4 = 80\text{ k}\Omega$ . What value of feedback resistor is needed to make it an averaging amplifier?