

Chapter 6, Problem 21.

Determine the equivalent capacitance at terminals *a* - *b* of the circuit in Fig. 6.55.

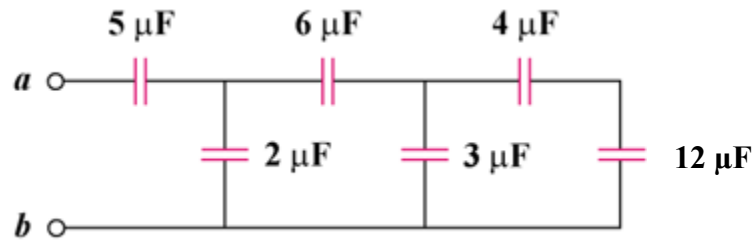


Figure 6.55
For Prob. 6.21.