

**Chapter 7, Problem 23.**

Consider the circuit in Fig. 7.103. Given that  $v_o(0) = 10$  V, find  $v_o$  and  $v_x$  for  $t > 0$ .

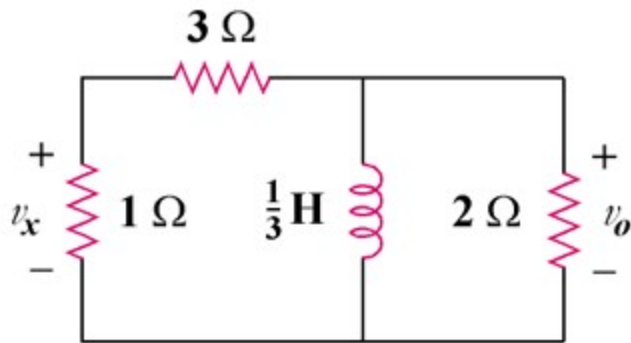


Figure 7.103  
For Prob. 7.23.