

Chapter 9, Problem 45.

Find current \mathbf{I}_o in the network of Fig. 9.52.

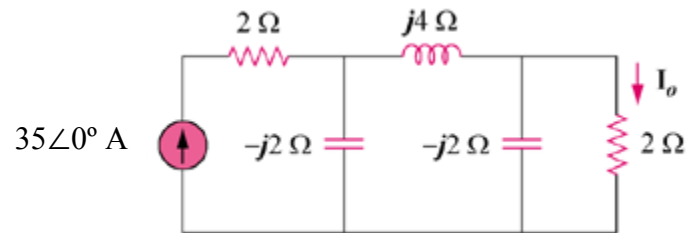


Figure 9.52
For Prob. 9.45.