

**Chapter 7, Problem 77.**

The switch in Fig. 7.141 opens at  $t = 0$ . Use *PSpice* to determine  $v(t)$  for  $t > 0$ .

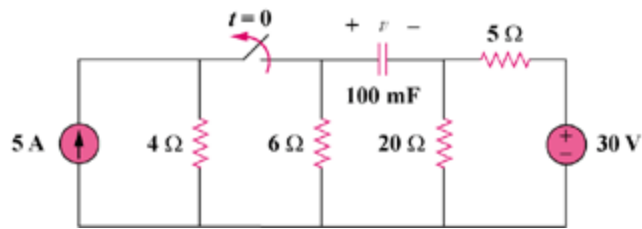


Figure 7.141  
For Prob. 7.77.