

Chapter 9, Problem 93.

A power transmission system is modeled as shown in Fig. 9.92. Given the source voltage and circuit elements

$V_s = 115\angle 0^\circ$ V, source impedance

$Z_s = (1 + j0.5) \Omega$, line impedance

$Z_l = (0.4 + j0.3) \Omega$, and load impedance

$Z_L = (23.2 + j18.9) \Omega$,

find the load current I_L .

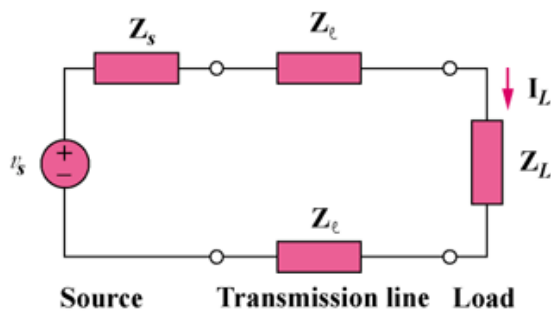


Figure 9.92
For Prob. 9.93.