

**Chapter 9, Problem 41.**

Find  $v(t)$  in the  $RLC$  circuit of Fig. 9.48.

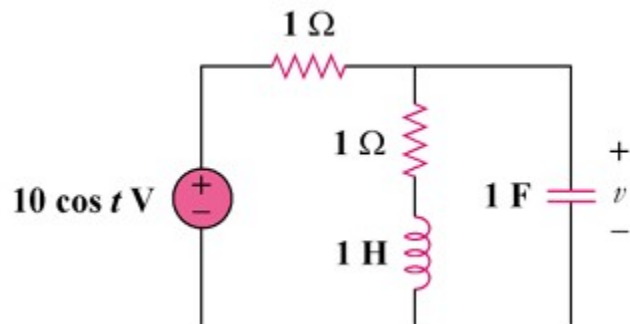


Figure 9.48  
For Prob. 9.41.