

Chapter 9, Problem 83.

An inductive bridge balances when $R_1 = 1.2 \text{ k}\Omega$, $R_2 = 500 \text{ }\Omega$, and $L_s = 250 \text{ mH}$.
What is the value of L_x , the inductance of the inductor under test?