

### Chapter 6, Solution 16

The equivalent capacitance at terminals  $a$ - $b$  in the circuit in Fig. 6.50 is  $30\ \mu\text{F}$ . Calculate the value of  $C$ .

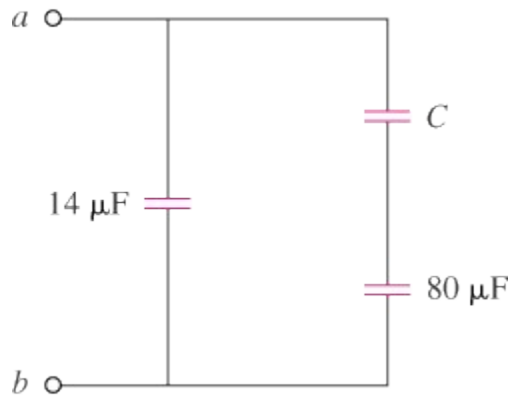


Figure 6.50  
For Prob. 6.16.

### Solution

$$C_{eq} = 14 + \frac{C \times 80}{C + 80} = 30 \rightarrow \underline{C = 20\ \mu\text{F}}$$