

Chapter 10, Problem 68.

For the circuit in Fig. 10.111, obtain the Thévenin equivalent at terminals a - b .

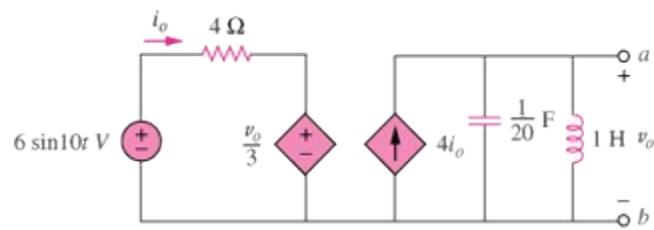


Figure 10.111
For Prob. 10.68.