## Chapter 6, Solution 30.

$$v_{o} = \frac{1}{C} \int_{0}^{t} i dt + i(0)$$
For  $0 < t < 1$ ,  $i = 90t$  mA,
$$v_{o} = \frac{10^{-3}}{3x10^{-6}} \int_{0}^{t} 90t dt + 0 = 15t^{2}kV$$

$$v_{o}(1) = 15 \text{ kV}$$
For  $1 < t < 2$ ,  $i = (180 - 90t)$  mA,
$$v_{o} = \frac{10^{-3}}{3x10^{-6}} \int_{1}^{t} (180 - 90t) dt + v_{o}(1)$$

$$= [60t - 15t^{2}]_{1}^{t} + 15kV$$

$$= [60t - 15t^{2} - (60 - 15) + 15] \text{ kV} = [60t - 15t^{2} - 30] \text{ kV}$$

$$v_{o}(t) = \begin{bmatrix} 15t^{2}kV, & 0 < t < 1 \\ [60t - 15t^{2} - 30]kV, & 1 < t < 2 \end{bmatrix}$$