

**Chapter 5, Problem 22**

Design an inverting amplifier with a gain of -15.