

**Chapter 7, Problem 70.**

Determine  $v_o$  for  $t > 0$  when  $v_s = 20$  mV in the op amp circuit of Fig. 7.135.

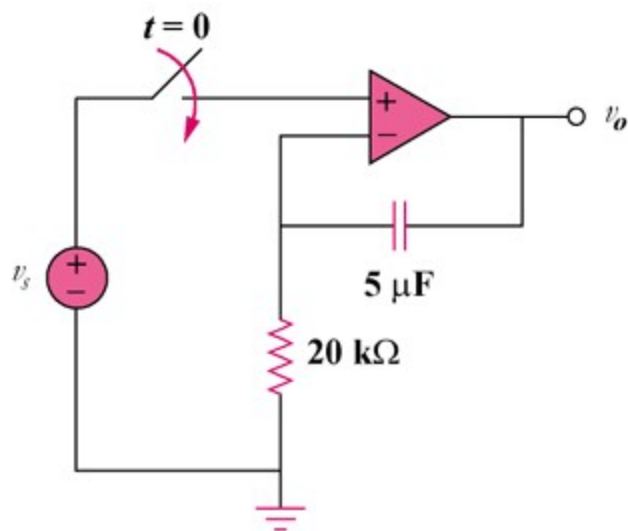


Figure 7.135  
For Prob. 7.70.