

### Chapter 5, Problem 29

Determine the voltage gain  $v_o/v_i$  of the op amp circuit in Fig. 5.67.

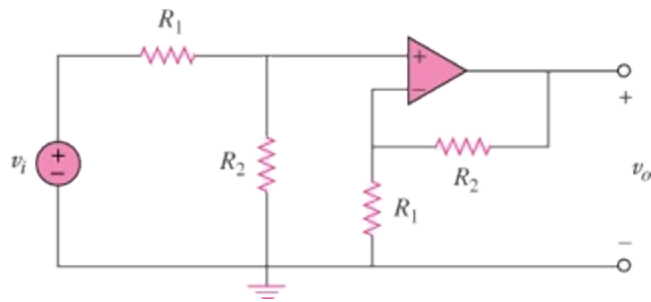


Figure 5.67  
For Prob. 5.29.