

Chapter 6, Solution 48.

Under steady-state dc conditions, find i and v in the circuit in Fig. 6.71.


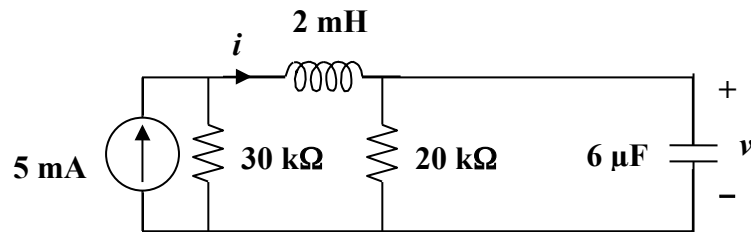


Figure 6.71
For Prob. 6.48.

Solution

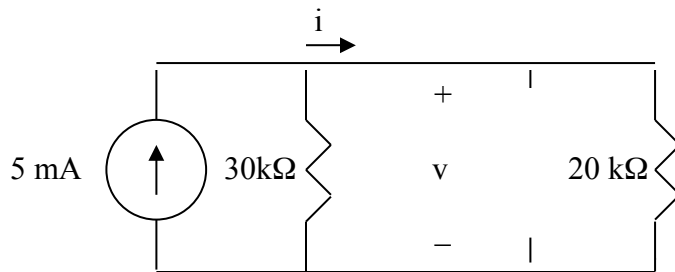Under steady-state, the inductor acts like a short-circuit, while the capacitor acts like an open circuit as shown below.



Using current division,

$$i = (30\text{k}/(30\text{k}+20\text{k}))(5\text{mA}) = \mathbf{3\text{ mA}}$$

$$v = 20\text{k}i = \mathbf{60\text{ V}}$$