

Chapter 10, Problem 76.

Determine \mathbf{V}_o and \mathbf{I}_o in the op amp circuit of Fig. 10.119.

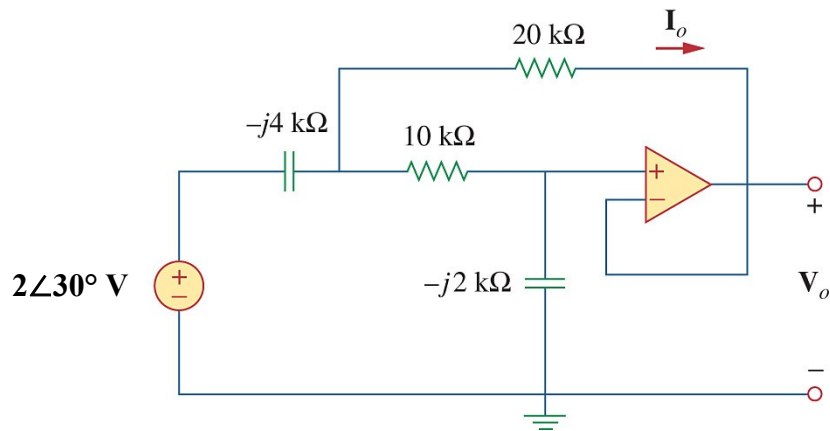


Figure 10.119
For Prob. 10.76.