

Chapter 7, Problem 75.

In the circuit of Fig. 7.140, find v_o and i_o , given that $v_s = 4 u(t)$ V and $v(0) = 1$ V.

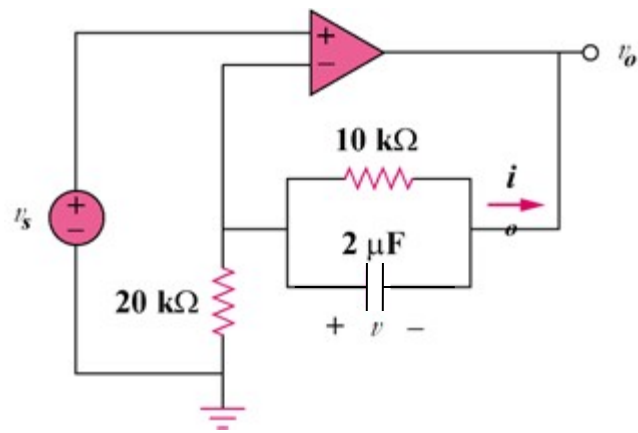


Figure 7.140
For Prob. 7.75.