

### Chapter 11, Solution 12.

For the circuit shown in Fig. 11.44, determine the load impedance  $Z$  for maximum power transfer (to  $Z$ ). Calculate the maximum power absorbed by the load.


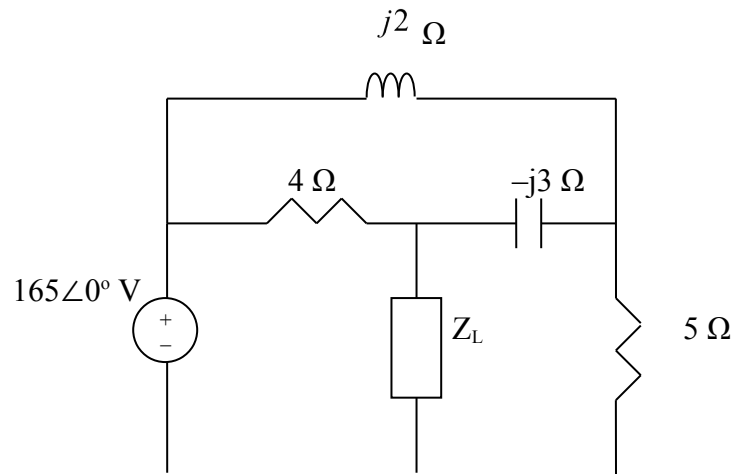


Figure 11.44  
For Prob. 11.12.
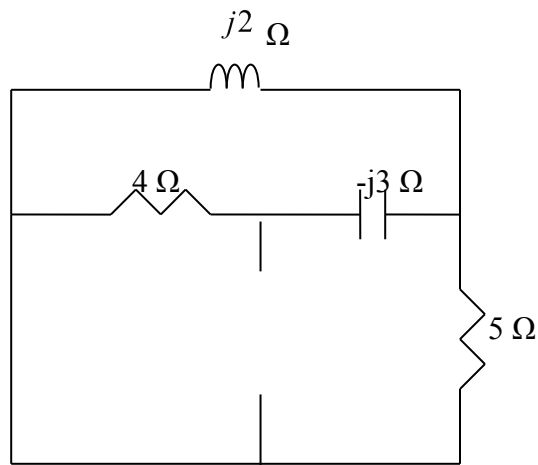
### Solution

We find the Thevenin impedance using the circuit below.




We note that the inductor is in parallel with the  $5\text{-}\Omega$  resistor and the combination is in series with the capacitor. That whole combination is in parallel with the  $4\text{-}\Omega$  resistor. Thus,

$$Z_{\text{Thev}} = \frac{4 \left( -j3 + \frac{5 \times j2}{5 + j2} \right)}{4 - j3 + \frac{5 \times j2}{5 + j2}} = \frac{4(0.6896 - j1.2758)}{4.69 - j1.2758} = \frac{4(1.4502 \angle -61.61^\circ)}{4.86 \angle -15.22^\circ}$$

$$= 1.1936 \angle -46.39^\circ$$

$$Z_{\text{Thev}} = 0.8233 - j0.8642 \text{ or } Z_L = [823.3 + j864.2] \text{ m}\Omega.$$

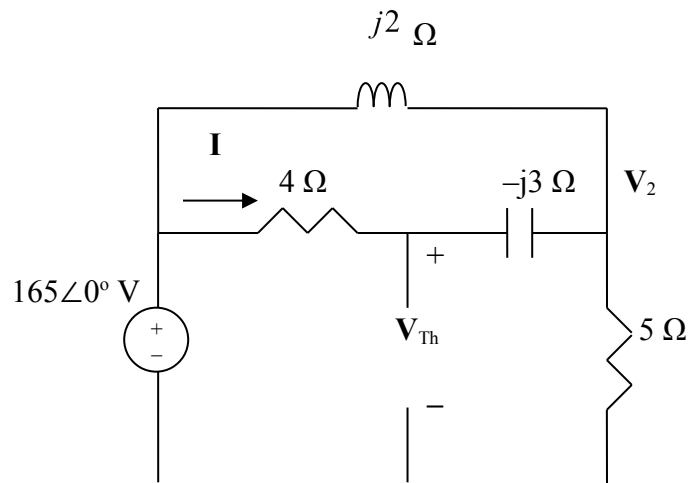We obtain  $V_{\text{Th}}$  using the circuit below. We apply nodal analysis.



$$\frac{V_2 - 165}{4 - j3} + \frac{V_2 - 165}{j2} + \frac{V_2 - 0}{5} = 0$$

$$(0.16 + j0.12 - j0.5 + 0.2)V_2 = (0.16 + j0.12 - j0.5)165$$

$$(0.5235 \angle -46.55^\circ)V_2 = (0.4123 \angle -67.17^\circ)165$$

4.125

$$\text{Thus, } V_2 = 129.94 \angle -20.62^\circ \text{ V} = 121.62 - j45.76$$

$$I = (165 - V_2)/(4 - j3) = (165 - 121.62 + j45.76)/(4 - j3)$$

$$= (63.06 \angle 46.52^\circ)/(5 \angle -36.87^\circ) = 12.613 \angle 83.39^\circ = 1.4519 + j12.529$$

$$V_{\text{Thev}} = 165 - 4I = 165 - 5.808 - j50.12 = [159.19 - j50.12] \text{ V}$$

$$= 166.89 \angle -17.48^\circ \text{ V}$$

We can check our value of  $V_{\text{Thev}}$  by letting  $V_1 = V_{\text{Thev}}$ . Now we can use nodal analysis to solve for  $V_1$ .

At node 1,

$$\frac{V_1 - 165}{4} + \frac{V_1 - V_2}{-j3} + \frac{V_2 - 0}{5} = 0 \rightarrow (0.25 + j0.3333)V_1 + (0.2 - j0.3333)V_2 = 41.25$$

At node 2,

$$\frac{V_2 - V_1}{-j3} + \frac{V_2 - 165}{j2} = 0 \rightarrow -j0.3333V_1 + (-j0.1667)V_2 = -j82.5$$

$$>> Y = [(0.25 + 0.3333i), -0.3333i; -0.3333i, (0.2 - 0.1667i)]$$

Y =

$$\begin{bmatrix} 0.2500 + 0.3333i & 0 - 0.3333i \\ 0 - 0.3333i & 0.2000 - 0.1667i \end{bmatrix}$$

$$>> I = [41.25; -82.5i]$$

I =

$$\begin{bmatrix} 41.2500 \\ 0 - 20.0000i \end{bmatrix}$$

$$>> V = \text{inv}(Y) * I$$

V =

$$\begin{bmatrix} 159.2221 - 50.1018i \\ 121.6421 - 45.7677i \end{bmatrix}$$

Please note, these values check with the ones obtained above.

To calculate the maximum power to the load,

$$|I_L| = (166.89 / (2 \times 0.8233)) = 101.34 \text{ A}$$

$$P_{\text{avg}} = [(|I_L|_{\text{rms}})^2 \times 0.8233] / 2 = \mathbf{4.228 \text{ mW}}.$$