

### Chapter 11, Problem 60.

For the circuit in Fig. 11.79, find  $V_o$  and the input power factor.

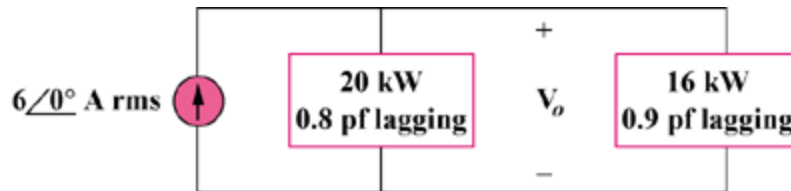


Figure 11.79  
For Prob. 11.60.