

Chapter 9, Problem 68.

Determine $\mathbf{Y_{eq}}$ for the circuit in Fig. 9.75.

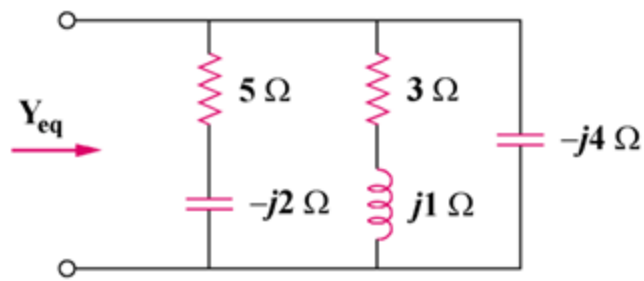


Figure 9.75
For Prob. 9.68.