Chapter 6, Solution 86.

$$V = V_R + V_L = Ri + L\frac{di}{dt} = 12x2te^{-10t} + 200x10^{-3}x(-20te^{-10t} + 2e^{-10t}) = (0.4 - 20t)e^{-10t} V$$