

Chapter 7, Problem 71.

For the op amp circuit in Fig. 7.136, suppose $v(0) = 0$ and $v_s = 3\text{V}$. Find $v(t)$ for $t > 0$.

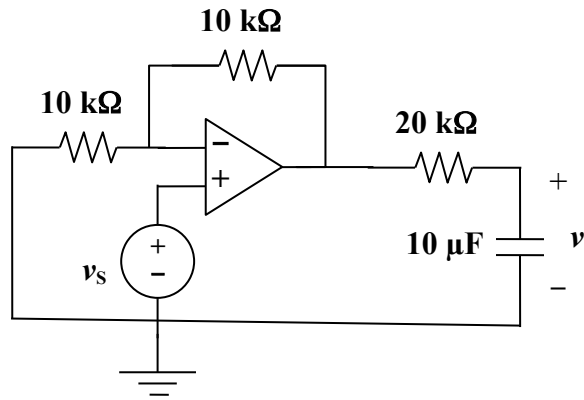


Figure 7.136
For Prob. 7.71.