

**Chapter 10, Problem 71.**

Find  $v_o$  in the op amp circuit shown in Fig. 114.

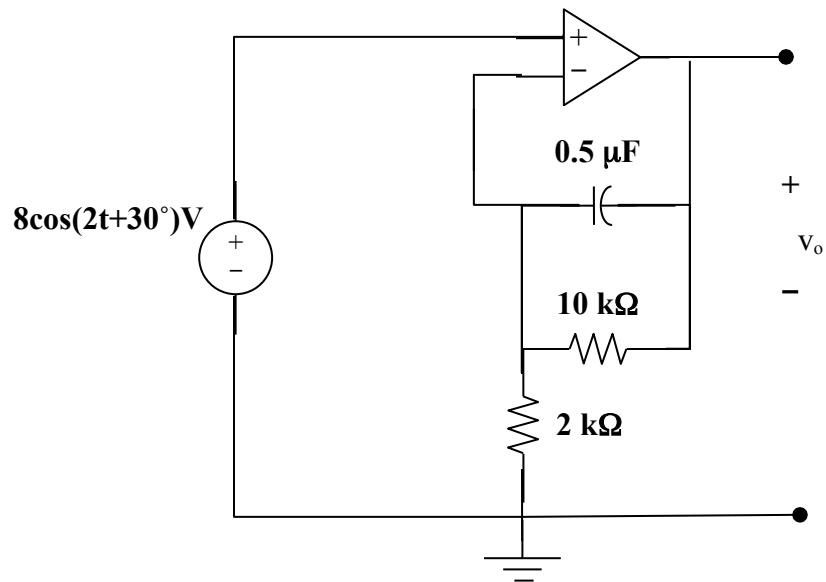


Figure 10.114  
For Prob. 10.71.