

Chapter 10, Solution 86.

The schematic is shown below. We insert three pseudocomponent PRINTs at nodes 1, 2, and 3 to print V_1 , V_2 , and V_3 , into the output file. Assume that $w = 1$, we set Total Pts = 1, Start Freq = 0.1592, and End Freq = 0.1592. After saving and simulating the circuit, we obtain the output file which includes:

		FREQ	VM(\$N_0002)	
	VP(\$N_0002)	1.592 E-01	6.000 E+01	3.000
E+01				
		FREQ	VM(\$N_0003)	
	VP(\$N_0003)	1.592 E-01	2.367 E+02	-8.483
E+01				
		FREQ	VM(\$N_0001)	
	VP(\$N_0001)	1.592 E-01	1.082 E+02	1.254
E+02				

Therefore,

$$V_1 = 60\angle 30^\circ \text{ V} \quad V_2 = 236.7\angle -84.83^\circ \text{ V} \quad V_3 = 108.2\angle 125.4^\circ \text{ V}$$

