

**Chapter 10, Problem 59.**

Calculate the output impedance of the circuit shown in Fig. 10.102.

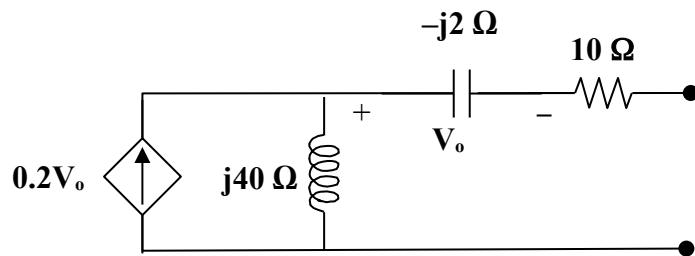


Figure 10.102  
For Prob. 10.59.