

Chapter 9, Problem 42.

Calculate $v_o(t)$ in the circuit in Fig. 9.49.

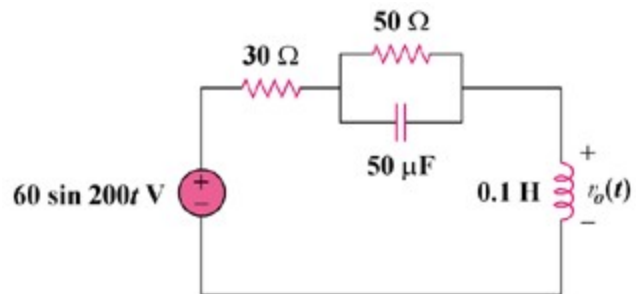


Figure 9.49
For Prob. 9.42.