

Chapter 11, Problem 12.

For the circuit shown in Fig. 11.44, determine the load impedance Z for maximum power transfer (to Z). Calculate the maximum power absorbed by the load.

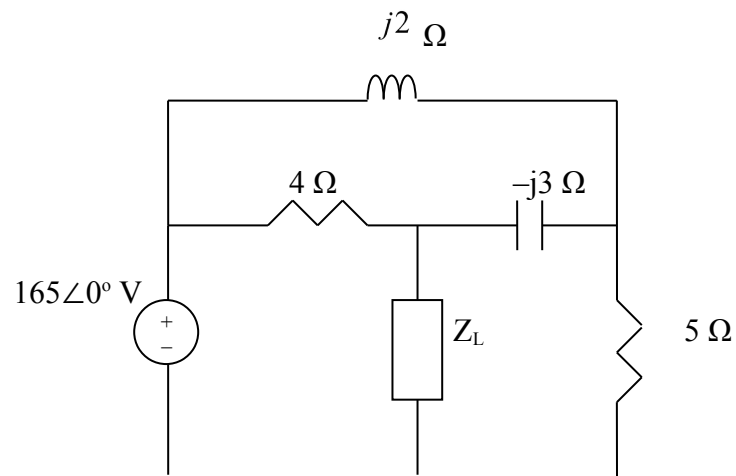


Figure 11.44
For Prob. 11.12.