

Chapter 9, Problem 61.

Find \mathbf{Z}_{eq} in the circuit of Fig. 9.68.

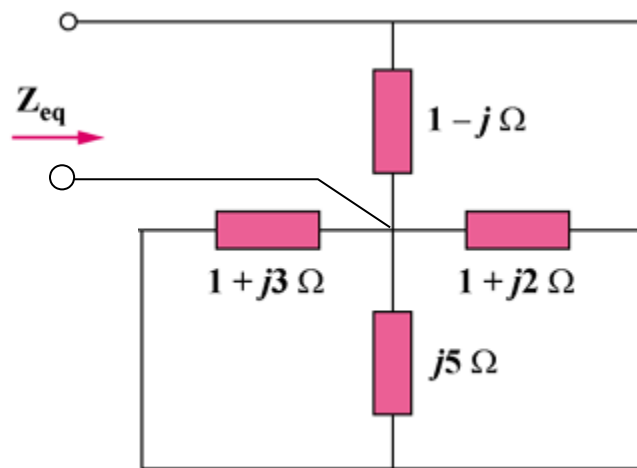


Figure 9.68
For Prob. 9.61.