

Chapter 6, Problem 9.

The current through a 0.5-F capacitor is $6(1 - e^{-t})$ A. Determine the voltage and power at $t=2$ s. Assume $v(0) = 0$.