

**Chapter 10, Problem 93.**

Fig. 10.135 shows a *Colpitts oscillator*. Show that the oscillation frequency is

$$f_o = 1/[2\pi\sqrt{LC_T}]$$

where  $C_T = (C_1 C_2)/(C_1 + C_2)$ . Assume  $R_i \gg X_{C2}$ .

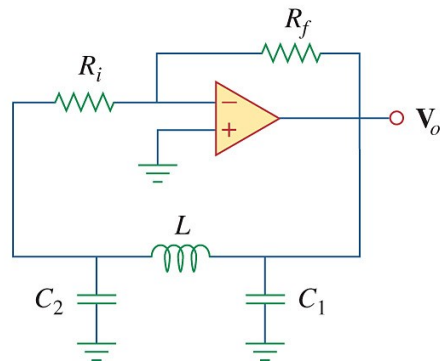


Figure 10.135  
For Prob. 10.93.