

*** Chapter 5, Problem 18.**

For the following circuit, solve for the Thevenin equivalent circuit looking into terminals A and B.

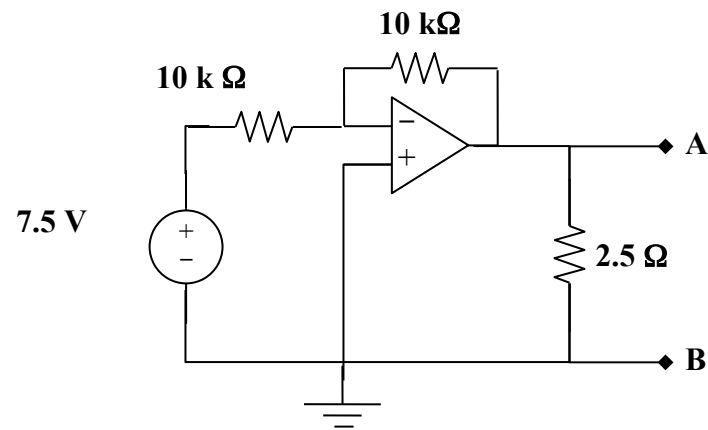


Figure 5.57
For Prob. 5.18.