

**Chapter 10, Problem 43.**

Using the superposition principle, find  $i_x$  in the circuit of Fig. 10.88.

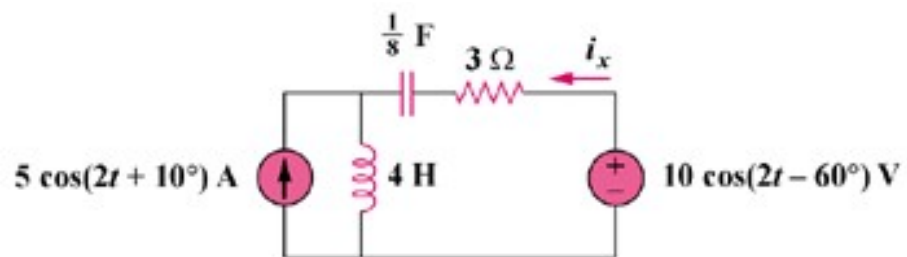


Figure 10.88  
For Prob. 10.43.