

Chapter 10, Problem 39.

Find \mathbf{I}_1 , \mathbf{I}_2 , \mathbf{I}_3 , and \mathbf{I}_x in the circuit in Fig. 10.84.

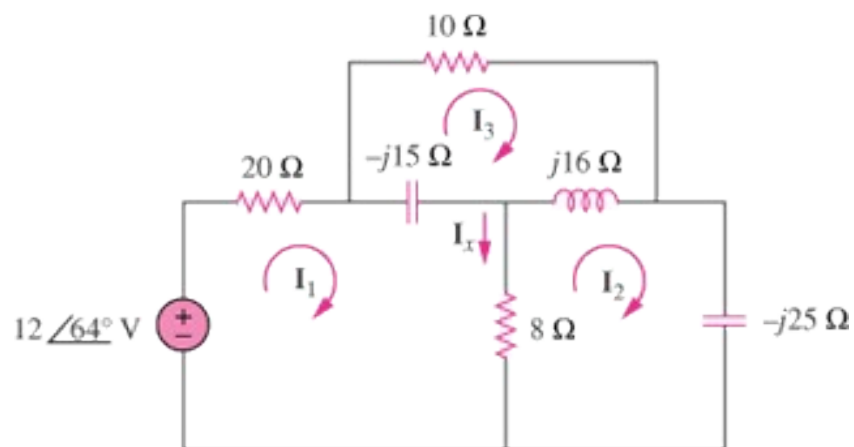


Figure 10.84
For Prob. 10.39.