

**Chapter 9, Problem 52.**

If  $\mathbf{V}_o = 8\angle 30^\circ$  V in the circuit of Fig. 9.59, find  $\mathbf{I}_s$ .

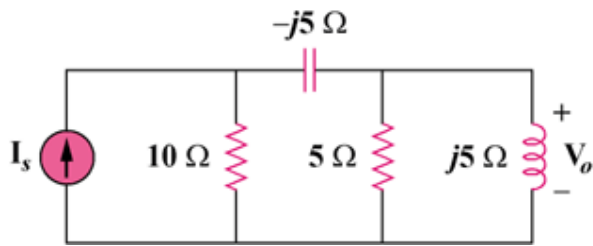


Figure 9.59  
For Prob. 9.52.