

**Chapter 6, Problem 57.**

Determine the  $L_{eq}$  that can be used to represent the inductive network of Fig. 6.79 at the terminals.

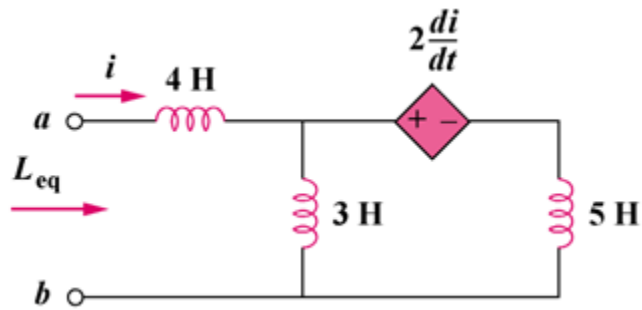


Figure 6.79  
For Prob. 6.57.