## Chapter 7, Problem 44.

The switch in Fig. 7.111 has been in position a for a long time. At t = 0, it moves to position b. Calculate i(t) for all t > 0.

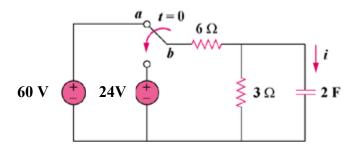


Figure 7.111 For Prob. 7.44.