

Chapter 9, Problem 31.

A series RLC circuit has $R=80\ \Omega$, $L=240\text{ mH}$, and $C = 5\text{mF}$. If the input voltage is $v(t)= 10 \cos(2t)\text{ V}$, find the current flowing through the circuit.