

Chapter 5, Problem 2

The open-loop gain of an op amp is 100,000. Calculate the output voltage when there are inputs of $+10\ \mu\text{V}$ on the inverting terminal and $+20\ \mu\text{V}$ on the noninverting terminal.