

**Chapter 6, Problem 29.**

Determine  $C_{eq}$  for each circuit in Fig. 6.61.

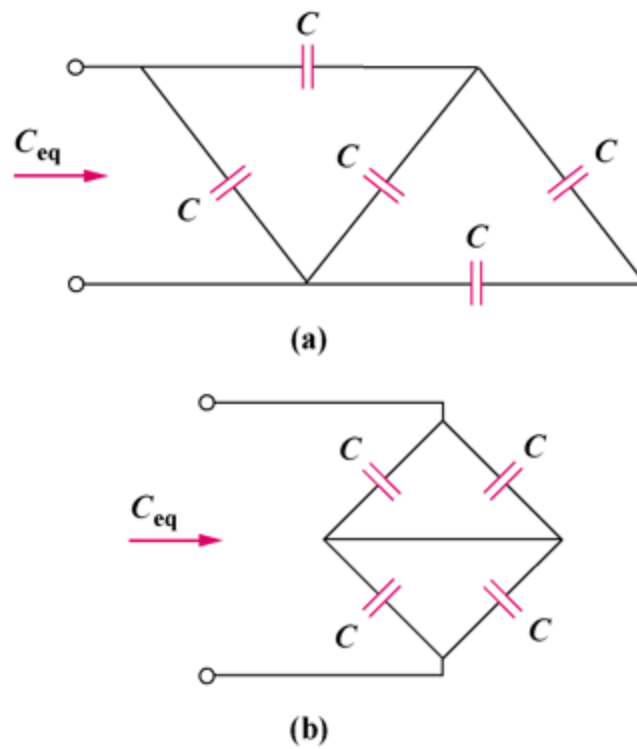


Figure 6.61  
For Prob. 6.29.