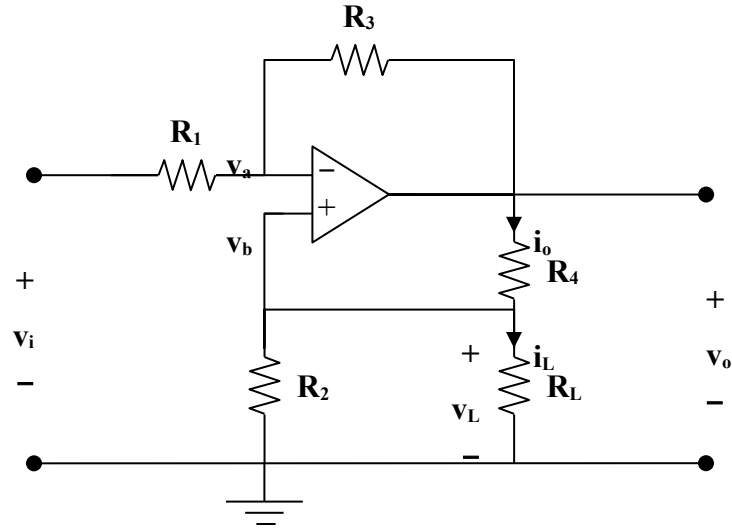


**Chapter 5, Solution 93.**



At node a,  $(v_i - v_a)/R_1 = (v_a - v_o)/R_3$

$$v_i - v_a = (R_1/R_3)(v_a - v_o)$$

$$v_i + (R_1/R_3)v_o = (1 + R_1/R_3)v_a \quad (1)$$

But  $v_a = v_b = v_L$ . Hence, (1) becomes

$$v_i = (1 + R_1/R_3)v_L - (R_1/R_3)v_o \quad (2)$$

$$i_o = v_o/(R_4 + R_2 \parallel R_L), \quad i_L = (R_2/(R_2 + R_L))i_o = (R_2/(R_2 + R_L))(v_o/(R_4 + R_2 \parallel R_L))$$

$$\text{Or,} \quad v_o = i_L[(R_2 + R_L)(R_4 + R_2 \parallel R_L)/R_2] \quad (3)$$

$$\text{But,} \quad v_L = i_L R_L \quad (4)$$

Substituting (3) and (4) into (2),

$$v_i = (1 + R_1/R_3) i_L R_L - R_1[(R_2 + R_L)/(R_2 R_3)](R_4 + R_2 \parallel R_L) i_L$$

$$= [((R_3 + R_1)/R_3)R_L - R_1((R_2 + R_L)/(R_2 R_3))(R_4 + (R_2 R_L)/(R_2 + R_L))] i_L$$

$$= (1/A) i_L$$

Thus,

$$A = \frac{1}{\left(1 + \frac{R_1}{R_3}\right)R_L - R_1 \left(\frac{R_2 + R_L}{R_2 R_3}\right) \left(R_4 + \frac{R_2 R_L}{R_2 + R_L}\right)}$$

Please note that A has the units of mhos. An easy check is to let every resistor equal 1-ohm and  $v_i$  equal to one amp. Going through the circuit produces  $i_L = 1A$ . Plugging into the above equation produces the same answer so the answer does check.