

### Chapter 5, Solution 65

Find  $v_o$  in the op amp circuit of Fig. 5.92.

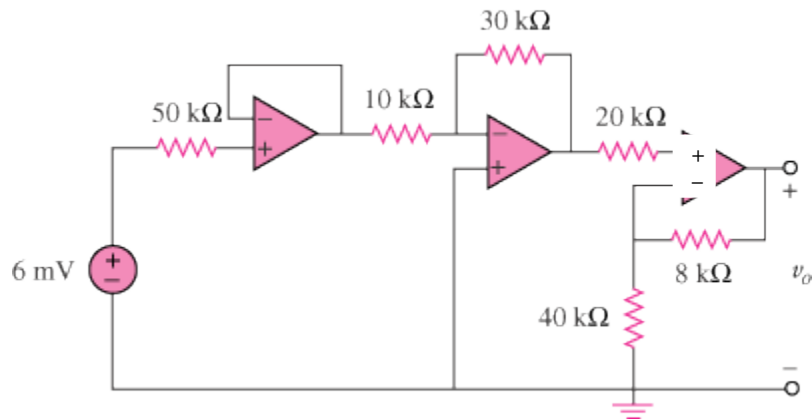


Figure 5.92  
For Prob. 5.65.

### Solution

The output of the first op amp (to the left) is 6 mV. The second op amp is an inverter so that its output is

$$v_o' = -\frac{30}{10}(6\text{mV}) = -18\text{ mV}$$

The third op amp is a noninverter so that

$$v_o' = \frac{40}{40+8} v_o \quad \longrightarrow \quad v_o = \frac{48}{40} v_o' = \underline{\underline{-21.6\text{ mV}}}$$