

Chapter 5, Solution 9.


(a) Let v_a and v_b be respectively the voltages at the inverting and noninverting terminals of the op amp

$$v_a = v_b = 4V$$

At the inverting terminal,

$$1\text{mA} = \frac{4 - v_o}{2\text{k}} \quad \mathbf{v_o = 2V}$$

(b)

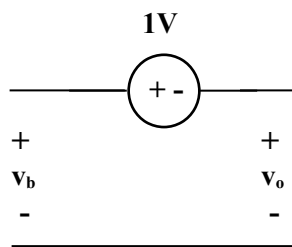

Since $v_a = v_b = 3V$,

$$-v_o + 1 + v_o = 0 \quad \longrightarrow \quad \mathbf{v_o = v_b - 1 = 2V}$$