

**Chapter 7, Problem 48.**

Find  $v(t)$  and  $i(t)$  in the circuit of Fig. 7.115.

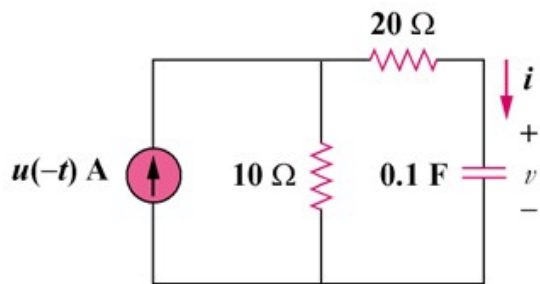


Figure 7.115  
For Prob. 7.48.