

### Chapter 11, Solution 69.

Refer to the circuit shown in Fig. 11.88.

- (a) What is the power factor?
- (b) What is the average power dissipated?
- (c) What is the value of the capacitance that will give a unity power factor when connected to the load?

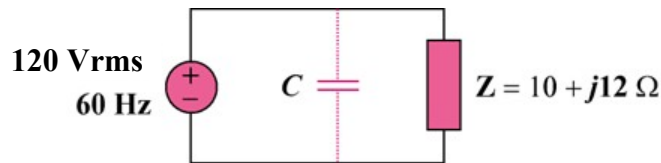


Figure 11.88  
For Prob. 11.69.

### Solution

- (a) Given that  $\mathbf{Z} = 10 + j12$
- $$\tan \theta = \frac{12}{10} \longrightarrow \theta = 50.19^\circ$$
- $$\text{pf} = \cos \theta = \mathbf{0.6402} = \mathbf{0.6402 \text{ (lagging)}}$$

- (b) 
$$\mathbf{S} = \frac{|\mathbf{V}|^2}{2\mathbf{Z}^*} = \frac{(120)^2}{(2)(10 - j12)} = 295.12 + j354.09$$
- The average power absorbed =  $P = \text{Re}(\mathbf{S}) = \mathbf{295.1 \text{ W}}$

- (c) For unity power factor,  $\theta_1 = 0^\circ$ , which implies that the reactive power due to the capacitor is  $Q_c = 354.09$

$$\text{But } Q_c = \frac{V^2}{2X_c} = \frac{1}{2}\omega C V^2$$

$$C = \frac{2Q_c}{\omega V^2} = \frac{(2)(354.09)}{(2\pi)(60)(120)^2} = \mathbf{130.4 \mu F}$$